

2023 Digital IC Design Homework 1

NAME	劉兆軒						
Student ID	N26112437						
Functional Simulation Result							
Stage 1	Pass/Fail	Stage 2	Pass/Fail	Stage 3	Pass/Fail	Stage 4	Pass/Fail
Stage 1							
<pre> -----Stage 1 : Maximum selection with 4-input MMS----- -----Stage 1 : Pass! ----- </pre>							
Stage 2							
<pre> -----Stage 2 : Minimum selection with 4-input MMS----- -----Stage 2 : Pass! ----- </pre>							
Stage 3							
<pre> -----Stage 3 : Maximum selection with 8-input MMS----- -----Stage 3 : Pass! ----- </pre>							
Stage 4							
<pre> -----Stage 4 : Minimum selection with 8-input MMS----- -----Stage 4 : Pass! ----- </pre>							
Description of your design							
<p>首先創建一個 combin module 用來判斷傳入的兩個 number 大小，再在 MMS_4num module 內呼叫 combin 函式分別將 number0,number1 和 number2,number3 比大小後再進行合併，而 MMS_8num module 同理。</p>							

```

module combin(n1,n2,sel,out);
    input [7:0] n1;
    input [7:0] n2;
    input sel;
    output[7:0] out;
    reg [7:0] out;
    reg [7:0] min;
    reg [7:0] max;
    reg cmp;
    always@(*)begin
        if(n1<n2)
            cmp = 1'b1;
        else
            cmp = 1'b0;
        case({sel,cmp})
            2'b00:
                out = n1;
            2'b01:
                out = n2;
            2'b10:
                out = n2;
            2'b11:
                out = n1;
        endcase
    end
endmodule

module MMS_4num(result, select, number0, number1, number2, number3);

    input        select;
    input  [7:0] number0;
    input  [7:0] number1;
    input  [7:0] number2;
    input  [7:0] number3;
    output [7:0] result;

    wire  [7:0]task1_out;
    wire  [7:0]task2_out;

    combin task1(number0,number1,select,task1_out);
    combin task2(number2,number3,select,task2_out);
    combin task3(task1_out,task2_out,select,result);

endmodule

module MMS_8num(result, select, number0, number1, number2, number3, number4, number5, number6, number7)

    input        select;
    input  [7:0] number0;
    input  [7:0] number1;
    input  [7:0] number2;
    input  [7:0] number3;
    input  [7:0] number4;
    input  [7:0] number5;
    input  [7:0] number6;
    input  [7:0] number7;
    output [7:0] result;

    wire  [7:0]result1;
    wire  [7:0]result2;

    MMS_4num task_a(result1, select, number0, number1, number2, number3);
    MMS_4num task_b(result2, select, number4, number5, number6, number7);
    combin task_c(result1,result2,select,result);

endmodule

combin task1(number0,number1,select,task1_out);
combin task2(number2,number3,select,task2_out);
combin task3(task1_out,task2_out,select,result);

```